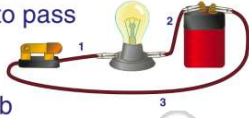




Name _____ Class _____ Date _____


1 What is the **function** of the **switch** shown in the diagram below?

- A it allows current to pass through it
- B it provides power for the bulb
- C it increases the voltage
- D it keeps the battery working



2 In the diagram below, if the bulb was **taken out** of the socket, how much **current** would pass through **point #1**?

- A all
- B most
- C some
- D none

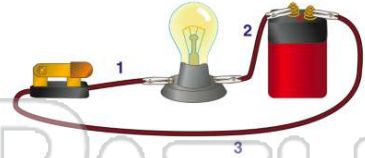


3 In the picture below, if the **battery** was replaced with a **newer** one with the same voltage on the label, one possible result would be _____.

- A the bulb burning out
- B the wire burning



4 What is the **cause of the lightning** in the diagram below?

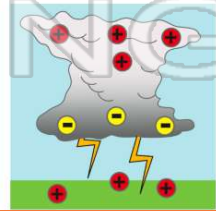- A rain
- B thunder
- C static electricity



PREVIEW

Please [Sign In](#) or [Sign Up](#) to download the printable version of this worksheet


7

- B protons
- C electrons
- D watts

- B no breaks in the electrical path
- C a battery
- D a switch


9 What is most **unsafe** about using an **electric drill** in this situation?

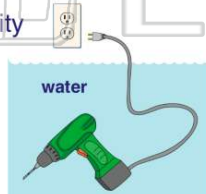- A working with electricity near water
- B using an electrical tool
- C getting wet
- D the drill will rust



10 Why is working with **electricity near water dangerous**?

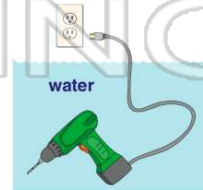- A it wastes energy
- B water creates extra resistance
- C water conducts electricity
- D water decreases electric current






ANSWER KEY

What is the **function** of the **switch** shown in the diagram below?

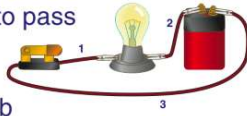
- A it allows current to pass through it
- B it provides power for the bulb
- C it increases the voltage
- D it keeps the battery working



(a)

In the diagram below, if the bulb was **taken out** of the socket, how much **current** would pass through **point #1**?

- A all
- B most
- C some
- D none

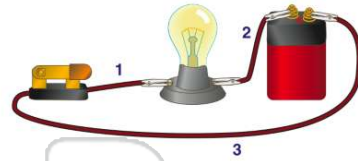

(d)

In the picture below, if the **battery** was replaced with a **newer** one with the same voltage on the label, one possible result would be _____.


- A the bulb burning out
- B the wire burning
- C the bulb looking brighter
- D



(c)

What is the **cause** of the **lightning** in the diagram below?

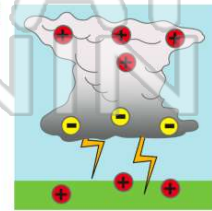- A rain
- B thunder
- C static electricity
- D increased resistance



(c)



PREVIEW


Please [Sign In](#) or [Sign Up](#) to download the printable version of this worksheet

D watts

D a switch

What is most **unsafe** about using an **electric drill** in this situation?

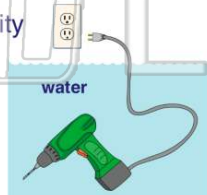- A working with electricity near water
- B using an electrical tool
- C getting wet
- D the drill will rust



(a)

Why is working with **electricity** near **water** **dangerous**?

- A it wastes energy
- B water creates extra resistance
- C water conducts electricity
- D water decreases electric current



(c)