




Name _____ Class _____ Date _____

1

A wire carries a current of **2.0 amperes**. How many **electrons** pass a **given point** in this wire in **1.0 second**?

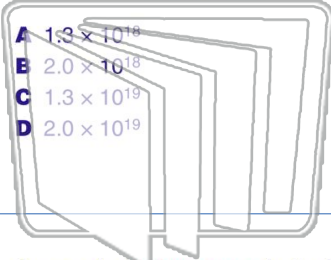- A 1.3×10^{18}
- B 2.0×10^{18}
- C 1.3×10^{19}
- D 2.0×10^{19}



2

In order to measure the current through an electrical device, an **ammeter** is placed in series with the device. **Compared to the electrical device, the ammeter should have a much**

- A lower permeability
- B higher permeability
- C lower resistance
- D higher resistance

3

A current of **3.0 amperes** is flowing in a circuit. How much **charge** passes a given point in the circuit in **30 seconds**?

4

Compared to the power dissipated in the **1.0-ohm** resistor, the **power dissipated** in the **3.0-ohm** resistor is

5




PREVIEW

Please [Sign In](#) or [Sign Up](#) to download the printable version of this worksheet

7

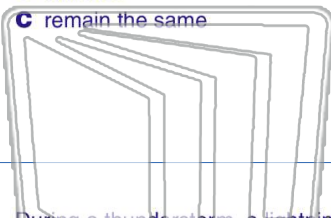- A decrease
- B increase
- C remain the same



the filament of the bulb **heats up**, its **resistance**

- A increases and the current through it decreases
- B increases and the current through it increases
- C decreases and the current through it decreases
- D decreases and the current through it increases



9

During a thunderstorm, a lightning strike transfers **12 coulombs** of charge in **2.0×10^{-3} second**. What is the **average current** produced in this strike?


- A 1.7×10^{-4} A
- B 2.4×10^{-2} A
- C 6.0×10^3 A
- D 9.6×10^3 A



10

How much **current** flows through a **12-ohm** flashlight bulb operating at **3.0 volts**?

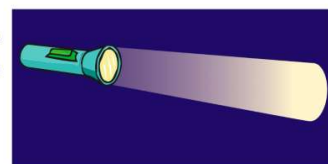- A 0.25 A
- B 0.75 A
- C 3.0 A
- D 4.0 A






Name _____ Class _____ Date _____


1 A wire carries a current of **2.0 amperes**. How many **electrons** pass a **given point** in this wire in **1.0 second**?

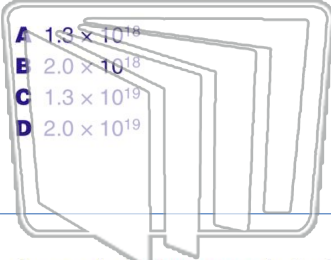- A 1.3×10^{18}
- B 2.0×10^{18}
- C 1.3×10^{19}
- D 2.0×10^{19}



2 In order to measure the current through an electrical device, an **ammeter** is placed in series with the device. Compared to the electrical device, the **ammeter** should have a much

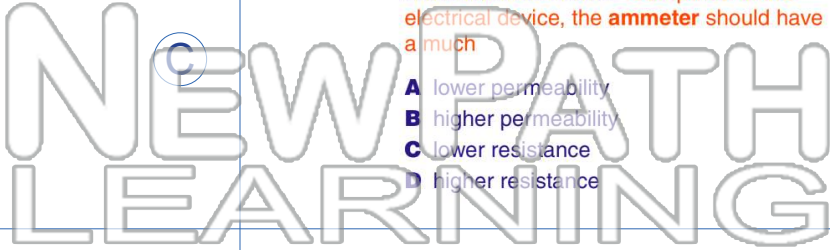- A lower permeability
- B higher permeability
- C lower resistance
- D higher resistance



3 A current of **3.0 amperes** is flowing in a circuit. How much **charge** passes a given point in the circuit in **30 seconds**?

4 Compared to the power dissipated in the **1.0-ohm** resistor, the **power dissipated** in the **3.0-ohm** resistor is




PREVIEW

Please [Sign In](#) or [Sign Up](#) to download the printable version of this worksheet

5

7

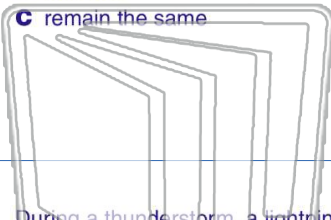- A decrease
- B increase
- C remain the same



the filament of the bulb **heats up**, its **resistance**

- A increases and the current through it decreases
- B increases and the current through it increases
- C decreases and the current through it decreases
- D decreases and the current through it increases



9 During a thunderstorm, a lightning strike transfers **12 coulombs** of charge in **2.0×10^{-3} second**. What is the **average current** produced in this strike?

- A 1.7×10^{-4} A
- B 2.4×10^{-2} A
- C 6.0×10^3 A
- D 9.6×10^3 A



10 How much **current** flows through a **12-ohm** flashlight bulb operating at **3.0 volts**?

- A 0.25 A
- B 0.75 A
- C 3.0 A
- D 4.0 A

